

EXIT TICKET: Reflective Journal # 4

Name: _____ Section: _____

Conduct simulations on current, resistance and EMF. From this, write a 5-sentence reflection from the activity you have done. Include your drawing of different circuit diagrams (Power Sources, Switches, Lamps, Resistors, Fuses, Ammeters and Voltmeters). Refer to this site:

<https://phet.colorado.edu/en/simulations/ohms-law>

Rewrite your answers here in your reflection journal.

EXIT TICKET: Reflective Journal # 4

Name: _____ Section: _____

Conduct simulations on current, resistance and EMF. From this, write a 5-sentence reflection from the activity you have done. Include your drawing of different circuit diagrams (Power Sources, Switches, Lamps, Resistors, Fuses, Ammeters and Voltmeters). Refer to this site:

<https://phet.colorado.edu/en/simulations/ohms-law>

Rewrite your answers here in your reflection journal.

EXIT TICKET: Reflective Journal # 4

Name: _____ Section: _____

Conduct simulations on current, resistance and EMF. From this, write a 5-sentence reflection from the activity you have done. Include your drawing of different circuit diagrams (Power Sources, Switches, Lamps, Resistors, Fuses, Ammeters and Voltmeters). Refer to this site:

<https://phet.colorado.edu/en/simulations/ohms-law>

Rewrite your answers here in your reflection journal.